



Introduction to SPICE

Acknowledgement

- These slides are adapted from the lecture: Spice Simulation by Prof. David Harris of Harvey Mudd College.

Introduction to SPICE

- **S**imulation **P**rogram with **I**ntegrated **C**ircuit **E**mphasis
 - Developed in 1970's at Berkeley
 - Many commercial versions are available
 - HSPICE is a robust industry standard
 - Has many enhancements that we will use
- Written in FORTRAN for punch-card machines
 - Circuits elements are called *cards*
 - Complete description is called a SPICE *deck*

Writing Spice Decks

- Writing a SPICE deck is like writing a good program
 - Plan: sketch schematic on paper or in editor
 - Modify existing decks whenever possible
 - Code: strive for clarity
 - Start with circuit name and its functionality
 - Generously comment
 - Test:
 - Predict what results should be
 - Compare with actual
 - *Garbage In, Garbage Out!*

Voltage Sources

- Node 0 is the ground terminal
- *DC Source*

Vname N1 N2 Type Value

Example:

```
vdd vdd 0 5
```

- *Piecewise Linear Source*

Vname N1 N2 PWL(T1 V1 T2 V2 T3 V3 ...)

Example:

```
Vin in 0 pw1 0ps 0 100ps 0 150ps 1.8 800ps 1.8
```


Voltage Sources...contd.

- *Pulsed Source*

V<name> N1 N2 PULSE V1 V2 td tr tf pw per

Example: Vin in gnd PULSE 0 5 0.5ns 0.1ns 0.1ns 4ns 8ns

PULSE v1 v2 td tr tf pw per

 

SPICE Elements


Letter	Element
R	Resistor
C	Capacitor
L	Inductor
K	Mutual Inductor
V	Independent voltage source
I	Independent current source
M	MOSFET
D	Diode
Q	Bipolar transistor
W	Lossy transmission line
X	Subcircuit
E	Voltage-controlled voltage source
G	Voltage-controlled current source
H	Current-controlled voltage source
F	Current-controlled current source

Units

Letter	Unit	Magnitude
a	atto	10^{-18}
f	femto	10^{-15}
p	pico	10^{-12}
n	nano	10^{-9}
u	micro	10^{-6}
m	milli	10^{-3}
k	kilo	10^3
x	mega	10^6
g	giga	10^9

Ex: 100 femptofarad capacitor = 100fF, 100f, 100e-15

Example: INV Circuit

 

- Each MOSFET has four terminals:
 - D (Drain)
 - G (Gate)
 - S (Source)
 - B (Body)
- The bulk terminal of **PMOS** should be tied to **Vdd**
- The bulk terminal of **NMOS** should be tied to **Ground**
- Each MOSFET has W (Width) and L (Length)

MOSFET Elements


M element for MOSFET

Mname drain gate source body type W=<width> L=<length>

Example:

m0 out in vdd vdd PMOS W=360nm L=180nm

m1 out in 0 0 NMOS W=180nm L=180nm

 

INV Circuit SPICE Deck

**

* Inverter SPICE deck

**

* Parameters and models

**

```
.include mosistsmc180.sp.txt
```

```
.options post list scale=1n
```

**

* Simulation netlist

**

```
Vdd Vdd 0 1.8V
```

```
Vin in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns
```

```
m0 out in Vdd Vdd PMOS W=360 L=180
```

```
m1 out in 0 0 NMOS W=180 L=180
```

```
Cload out 0 0.01pF
```

**


* Stimulus and plot statements

**

```
.tran 1n 40n
```

```
.plot V(in) V(out)
```

```
.end
```

 


Running HSPICE


- Run from Command Line
prompt% hspice -i inv.sp -o inv.lis
- When the job finishes, HSPICE displays:
>info: ***** hspice job concluded

SPICE Explorer

prompt% sx

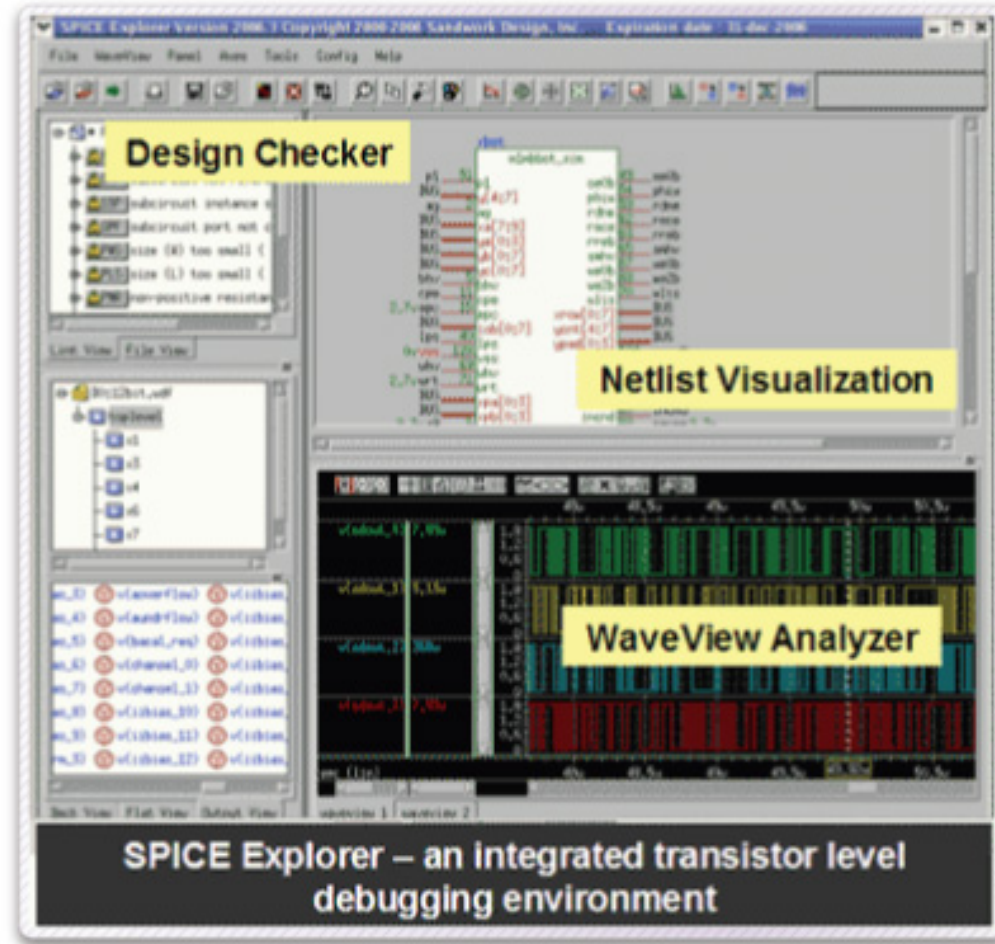

Viewing Waveforms

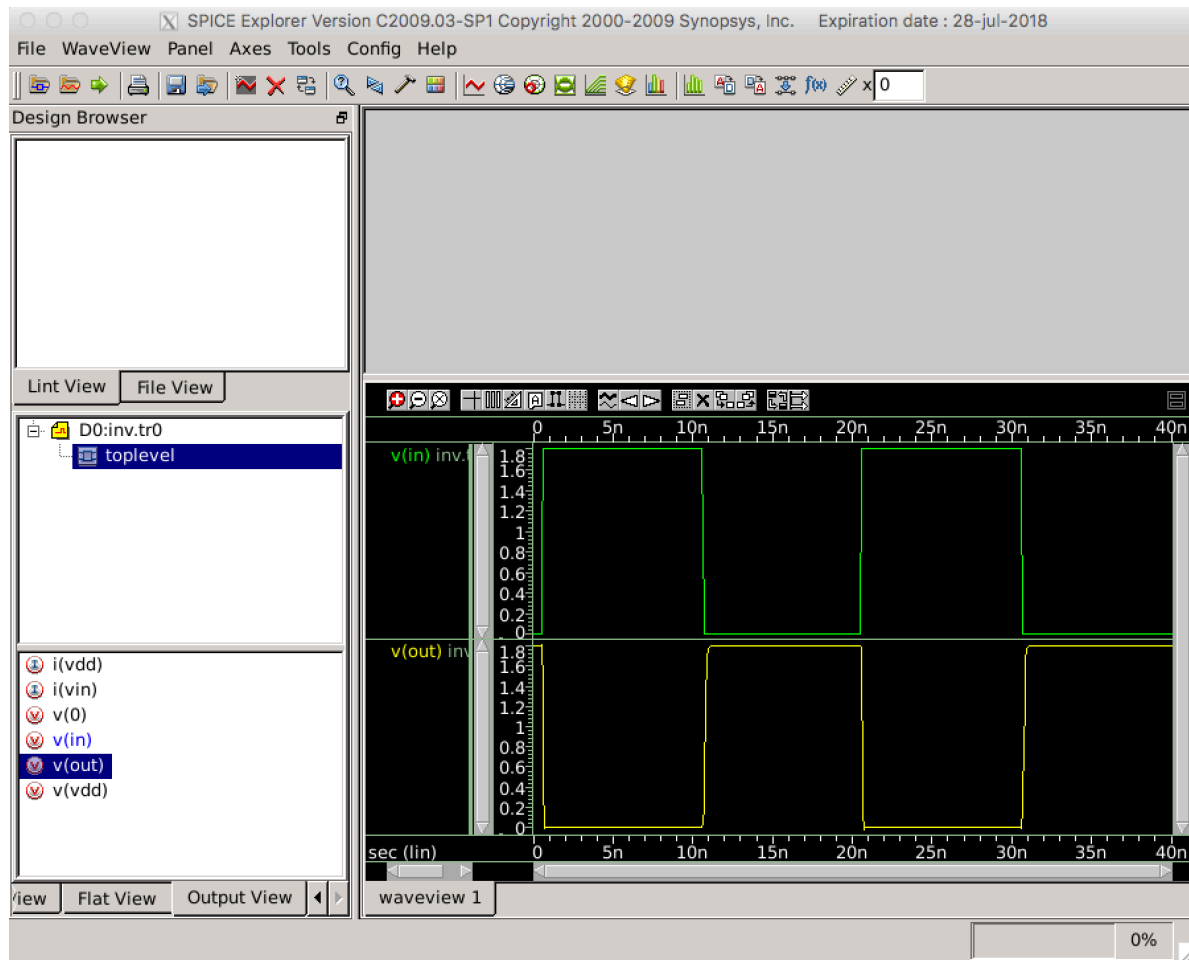

Getting Started

- ☐ Connect to USF RC Research Cluster
- ☐ Setup path by editing `.bashrc` file
- ☐ Copy inverter and model files
- ☐ Run **hspice**
- ☐ Run **sx**
- ☐ Print the waveforms to a file