

CDA 4213 001L/CIS 6930 012
Fall 2019
CMOS VLSI Design

Lab 2 Report

Canvas Submission
Due: 11:59 PM, 22nd Sept. 2019


Note: Upload PDF version of this report. Only PDF format is accepted.

Today's Date:	9/11/19
Your Name:	Boyang Wu
Your U Number:	U95035892
No. of Hours Spent:	4
Exercise Difficulty: (Easy, Average, Hard)	Average
Any Other Feedback:	Took a while to figure out parts 1 and 2 (which are really the easiest) but everything was fine after that.

Question 1 (5 pts): NMOS Transistor

Include the following

a) Transistor level diagram

 

b) Spice netlist (.sp file contents)

```
GNU nano 2.0.9 File: nmos.sp
**-----
* Inverter SPICE deck
**-----
* Parameters and models
**-----
.include mosistsmc180.sp.txt
.options post list scale=1n

**-----
* Simulation netlist
**-----
Vdd Vdd 0 1.8V
*Vin in 0 PWL(0 0 10ns 0 11ns 1.8 20ns 1.8)
Vin in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns


m0 out Vdd in Vdd NMOS W=180 L=180
*m1 out 0 in 0 PMOS W=180 L=180

*Cload out 0 0.01pF

.tran 1ns 40ns
.measure tran tr TRIG v(out) val=0.36 RISE=1 TARG v(out) val=1.44 RISE=1
.measure tran tf TRIG v(out) val=1.44 FALL=1 TARG v(out) val=0.36 FALL=1
.measure tran tpdr TRIG v(in) val=0.9 FALL=1 TARG v(out) val=0.9 RISE=1
.measure tran tpdf TRIG v(in) val=0.9 RISE=1 TARG v(out) val=0.9 FALL=1

*** Output Statements
.plot V(in) V(out)
.end
```

c) Waveform results

 

d) Explain how you demonstrate that NMOS transistor is good (poor) conductor of 0 (1).

When V_{in} goes to 1.8V, V_{out} only goes to 1.65V \rightarrow degraded 1.8V or 1


When V_{in} goes to 0V, V_{out} goes to 0V \rightarrow strong 0

Question 2 (5 pts): PMOS Transistor

Include the following

a) Transistor level diagram

pMOS

 

b) Spice netlist (.sp file contents)

```
GNU nano 2.0.9 File: pmos.sp
**-----
* Inverter SPICE deck
**-----
* Parameters and models
**-----
.include mosistsmc180.sp.txt
.options post list scale=1n
**-----
* Simulation netlist
**-----
Vdd Vdd 0 1.8V
*Vin in 0 PWL(0 0 10ns 0 11ns 1.8 20ns 1.8)
Vin in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns


*m0 out Vdd in Vdd NMOS W=180 L=180
m1 out 0 in 0 PMOS W=180 L=180

*Clod out 0 0.01pF

.tran 1ns 40ns
.measure tran tr TRIG v(out) val=0.36 RISE=1 TARG v(out) val=1.44 RISE=1
.measure tran tf TRIG v(out) val=1.44 FALL=1 TARG v(out) val=0.36 FALL=1
.measure tran tpdr TRIG v(in) val=0.9 FALL=1 TARG v(out) val=0.9 RISE=1
.measure tran tpdf TRIG v(in) val=0.9 RISE=1 TARG v(out) val=0.9 FALL=1

*** Output Statements
.plot V(in) V(out)
.end
```

c) Waveform results

 

d) Explain how you demonstrate that PMOS transistor is good (poor) conductor of 0 (1).


When V_{in} goes to 1.8V, V_{out} goes to 1.8V -> strong 1.8V or 1

When V_{in} goes to 0V, V_{out} goes to 0.2V -> degraded 0

Question 3 (10 pts): Transmission Gate

Include the following

a) Transistor level diagram

 

b) Spice netlist (.sp file contents)

```
GNU nano 2.0.9 File: tgate.sp
**-----
* Inverter SPICE deck
**-----
* Parameters and models
**-----
.include mosistsmc180.sp.txt
.options post list scale=1n

**-----
* Simulation netlist
**-----
Vdd Vdd 0 1.8V
*Vin in 0 PWL(0 0 10ns 0 11ns 1.8 20ns 1.8)
Vin in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns


m0 out Vdd in Vdd NMOS W=180 L=180
m1 out 0 in 0 PMOS W=180 L=180

*Clload out 0 0.01pF

.tran 1ns 40ns
.measure tran tr TRIG v(out) val=0.36 RISE=1 TARG v(out) val=1.44 RISE=1
.measure tran tf TRIG v(out) val=1.44 FALL=1 TARG v(out) val=0.36 FALL=1
.measure tran tpdr TRIG v(in) val=0.9 FALL=1 TARG v(out) val=0.9 RISE=1
.measure tran tpdf TRIG v(in) val=0.9 RISE=1 TARG v(out) val=0.9 FALL=1

*** Output Statements
.plot V(in) V(out)
.end
```

c) Waveform results

 

d) Explain how you demonstrate that the transmission gate is good conductor of both 1 and 0.


When V_{in} goes to 1.8V, V_{out} goes to 1.8V -> strong 1.8V or 1

When V_{in} goes to 0V, V_{out} goes to 0V -> strong 0

Question 4 (10 pts): 2-input Multiplexor

Include the following

a) Transistor level diagram

 

b) Spice netlist (.sp file contents)

```

GNU nano 2.0.9                               File: mux.sp
**-----
* Inverter SPICE deck
**-----
* Parameters and models
**-----
.include mosistsmc180.sp.txt
.options post list scale=1n

**-----
* Simulation netlist
**-----
Vdd Vdd 0 1.8V

*Vname N1 N2 PWL(T1 V1 T2 V2 T3 V3)
*Vin  in 0 PWL(0 0 10ns 0 11ns 1.8 20ns 1.8)

*Vname N1 N2 PULSE V1 V2 td tr tf pw per
Vin  in 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 10ns 20ns
Vin1 in1 0 PULSE 0 1.8V 0.5ns 0.1ns 0.1ns 5ns 10ns
Vin2 in2 0 PULSE 0 1.8V 3.0ns 0.1ns 0.1ns 5ns 10ns

*m# drain gate source body XMOS W=#nm L=#nm

*Transmission gate D0
m0 out N in1 Vdd NMOS W=180 L=180
m1 out in in1 0 PMOS W=180 L=180

*Transmission gate D1
m2 out in in2 Vdd NMOS W=180 L=180
m3 out N in2 0 PMOS W=180 L=180

*Inverter for input
m4 N in Vdd Vdd PMOS W=180 L=180
m5 N in 0 0 NMOS W=180 L=180


*Clload out 0 0.01pF

.tran 1ns 40ns
.measure tran tr TRIG v(out) val=0.36 RISE=1 TARG v(out) val=1.44 RISE=1
.measure tran tf TRIG v(out) val=1.44 FALL=1 TARG v(out) val=0.36 FALL=1
.measure tran tpdr TRIG v(in) val=0.9 FALL=1 TARG v(out) val=0.9 RISE=1
.measure tran tpdf TRIG v(in) val=0.9 RISE=1 TARG v(out) val=0.9 FALL=1

*** Output Statements
.plot V(in) V(out)
.end

```

c) Waveform results

 

1st row – V(in) or Mux selector (S)

2nd row – V(in1) or D0

3rd row – (Vin2) or D1

4th row – (Vout) or Y

As you can see, when the selector (Vin) is high (1.8V) only V(in2) input will go to V(out). When selector is low (0V) only V(in1) input will go to V(out)