

CDA 4213 001/CIS 6930 012
Fall 2019
CMOS VLSI Design

Lab 5 Report

Canvas Submission
Due: 11:59 PM, 20th Oct. 2019

You need to submit only report for your team.

Note: Upload PDF version of this report. Only PDF format is accepted.


Today's Date:	10-19-19
Your Team and U Numbers:	Trent Callahan - U14228486 Denislav Tsonev - U64519666 Boyang Wu - U95035892
Your U Number:	U14228486
No. of Hours Spent:	30
Exercise Difficulty: (Easy, Average, Hard)	Hard
Work Distribution: (Identify who did what)	Boyang - D Flip-Flop and 3-Bit Shift Register design and layout Denislav - D Latch design and layout Trent - Lab report, unused NAND-based D Latch
Any Other Feedback:	

Question 1 (5 pts): Positive Level Sensitive D-latch


Include the following

- a) Transistor level diagram
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

Transistor Level Diagram -

 


Layout image -

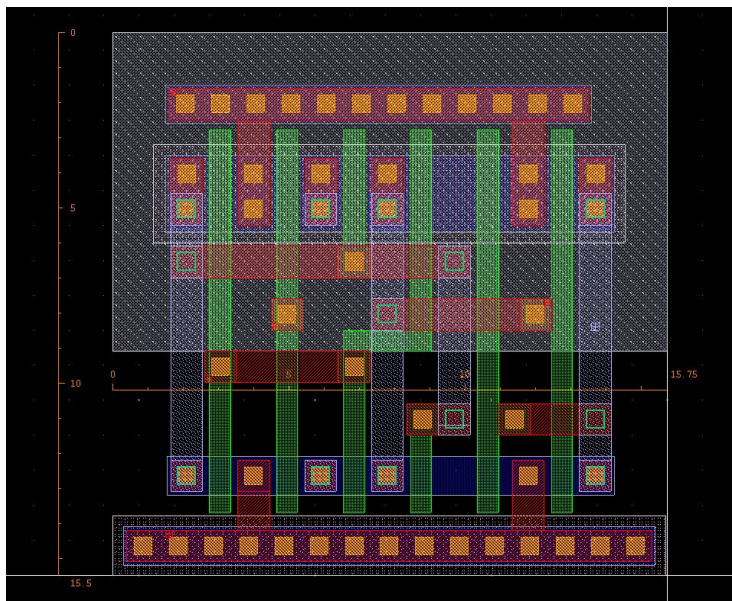

Bounding Box Area -

$$15.5 * 15.75 = 244.125$$

Waveform Results -

 


Question 2 (5 pts): Positive Edge Triggered D Flip-flop


Include the following

- Transistor level diagram
- Image of your layout
- Bounding box area (width x height)
- Waveform results

Transistor Level Diagram -

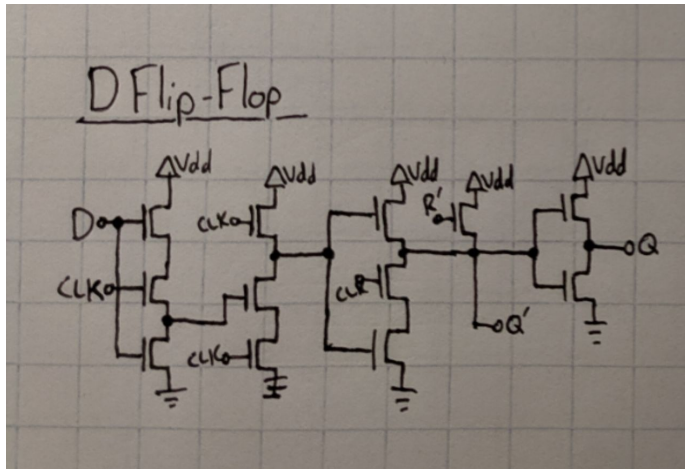

Layout Image -

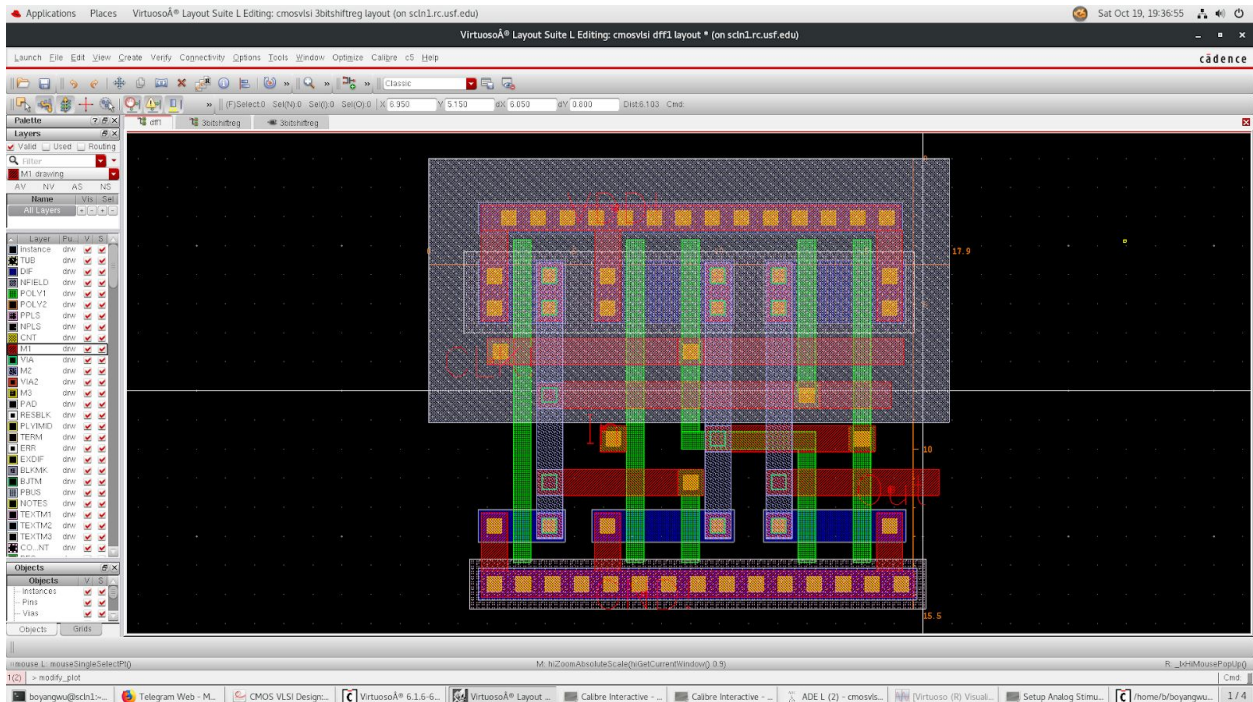

Bounding Box Area -

$$15.5 * 17.9 = 277.45$$

Waveform Results -




Question 3 (10 pts): 3-bit Shift Register


Include the following

- Transistor level diagram
- Image of your layout
- Bounding box area (width x height)
- Waveform results

Transistor Level Diagram -

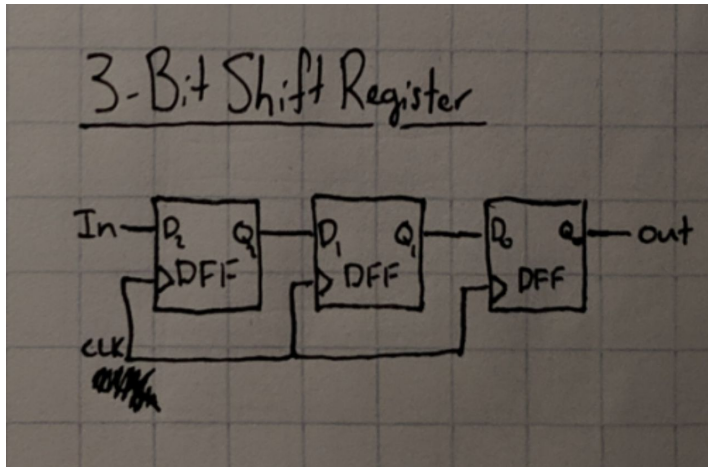

Layout Image -

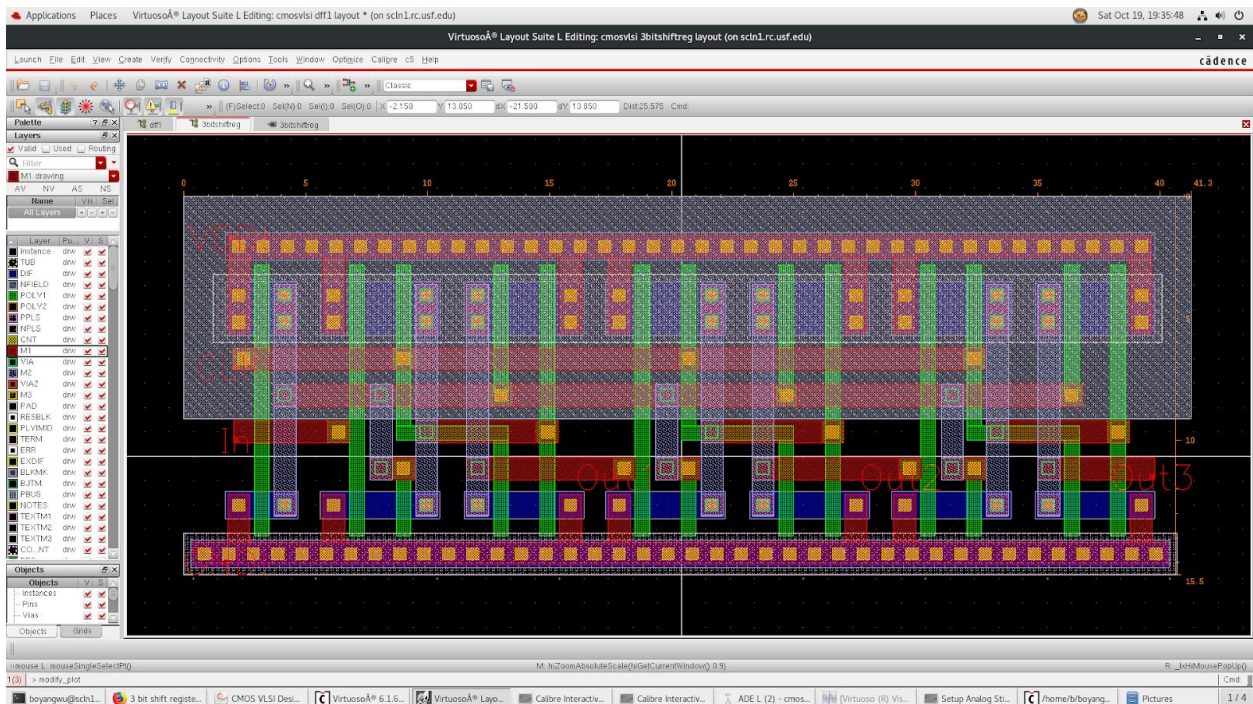

Bounding Box Area -

$$41.3 * 15.5 = 640.15$$

Waveform Results -

