

CDA 4213 001/CIS 6930 012
Fall 2019
CMOS VLSI Design

Lab 3 Report

Canvas Submission
Due: 11:59 PM, Sunday, 29th Sept. 2019

You need to submit only report for your team.

Note: Upload PDF version of this report. Only PDF format is accepted.

Today's Date:	9/26/19
Your Team and U Numbers:	Trent Callahan U14228486 Denislav Tsonev U64519666 Boyang Wu U95035892
Your U Number:	U14228486
No. of Hours Spent:	15
Exercise Difficulty: (Easy, Average, Hard)	Average
Work Distribution: (Identify who did what)	Denislav - Designed NAND gate Boyang - Designed NOR gate, reduced sizes for all gates Trent - Debugging and Report
Any Other Feedback:	Tell us how to import NMOS/PMOS from C5 library earlier

Question 1 (10 pts): Inverter

Include the following

- a) Transistor level diagram
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

Transistor level diagram -


 


Image of layout -

 

Bounding box area -

$$7 * 6.5 = 45.5$$

Waveform results -



Question 2 (10 pts): 2-input NAND

Include the following

- a) Transistor level diagram
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

Transistor level diagram -


 



Image of layout -

 

Bounding box area -

$$8.1 * 8.6 = 69.66$$

Waveform results -

 

Question 3 (10 pts): 2-input NOR

Include the following

- a) Transistor level diagram
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

Transistor level diagram -


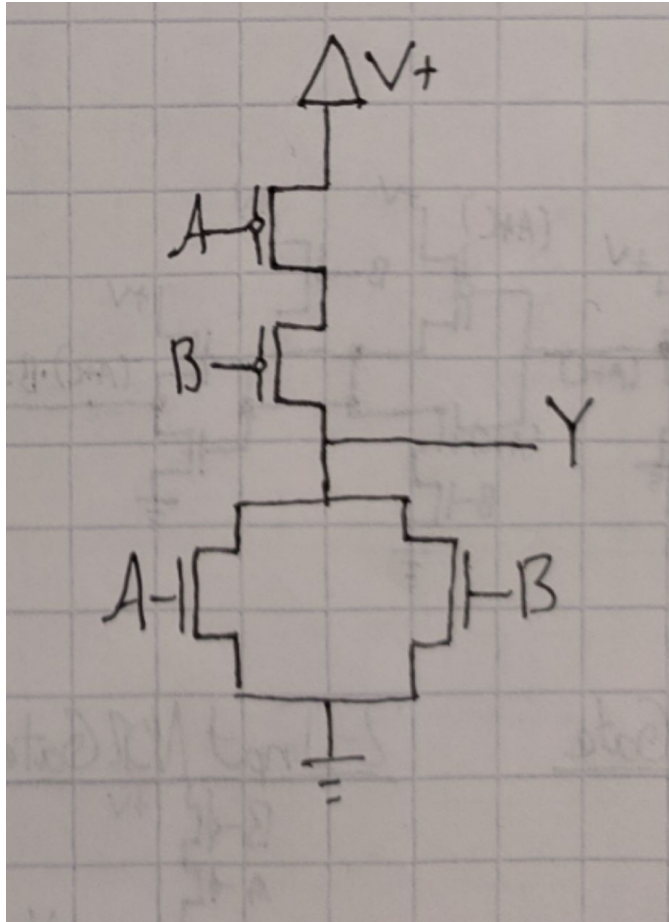


Image of layout -

 

Bounding box area -

$$8 * 8.6 = 68.8$$

Waveform results -

