

**CDA 4213 001/CIS 6930 012**  
**Fall 2019**  
**CMOS VLSI Design**

**Lab 3 Report**

**Canvas Submission**  
**Due: 11:59 PM, Sunday, 29th Sept. 2019**

You need to submit only report for your team.

Note: Upload PDF version of this report. Only PDF format is accepted.


Today's Date:	9/26/19
Your Team and U Numbers:	Trent Callahan U14228486 Denislav Tsonev U64519666 Boyang Wu U95035892
Your U Number:	U95035892
No. of Hours Spent:	20
Exercise Difficulty: (Easy, Average, Hard)	Average
Work Distribution: (Identify who did what)	Denislav - Designed NAND gate Boyang - Designed NOR gate, reduced sizes for all gates Trent - Debugging and Report
Any Other Feedback:	Tell us how to import NMOS/PMOS from C5 library earlier

### Question 1 (10 pts): Inverter


Include the following

- a) Transistor level diagram
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

#### Transistor level diagram -

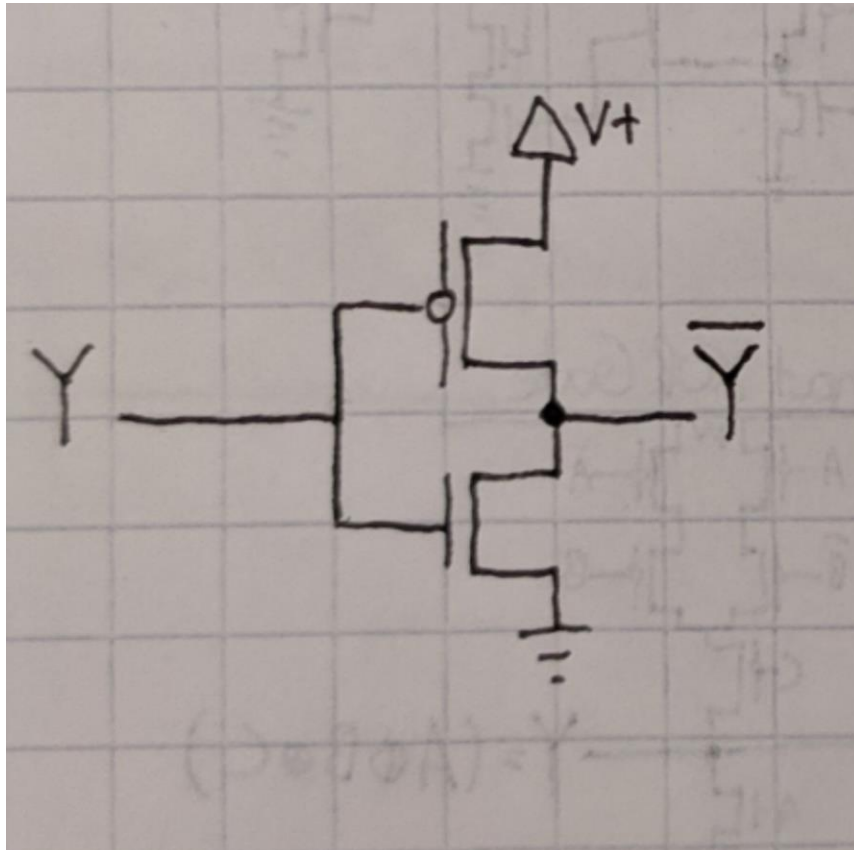


**Image of layout -**

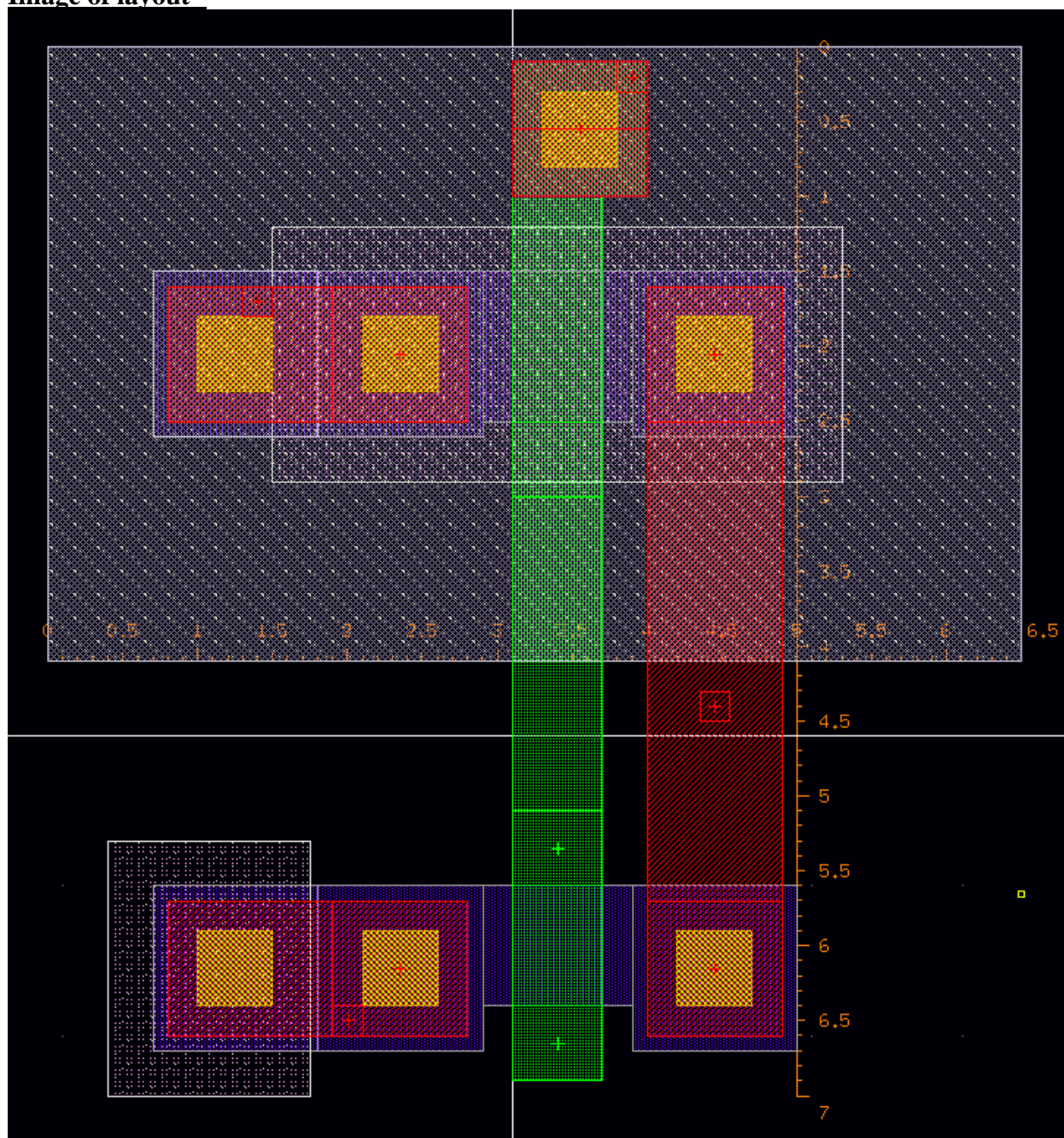

**Bounding box area -**

$$7 * 6.5 = 45.5$$

## Waveform results -

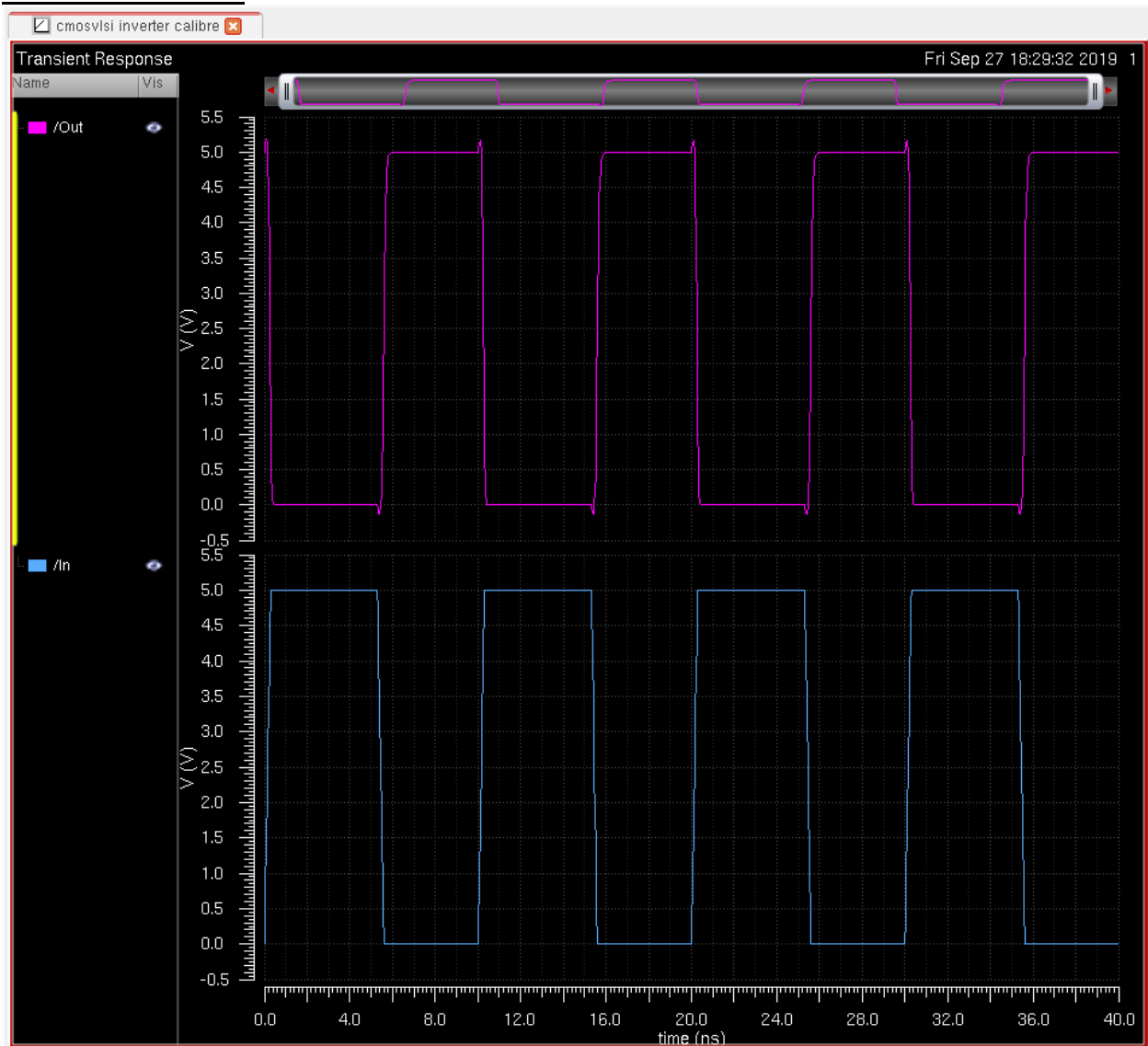

**Question 2 (10 pts): 2-input NAND**

Include the following

- a) Transistor level diagram
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

**Transistor level diagram -**


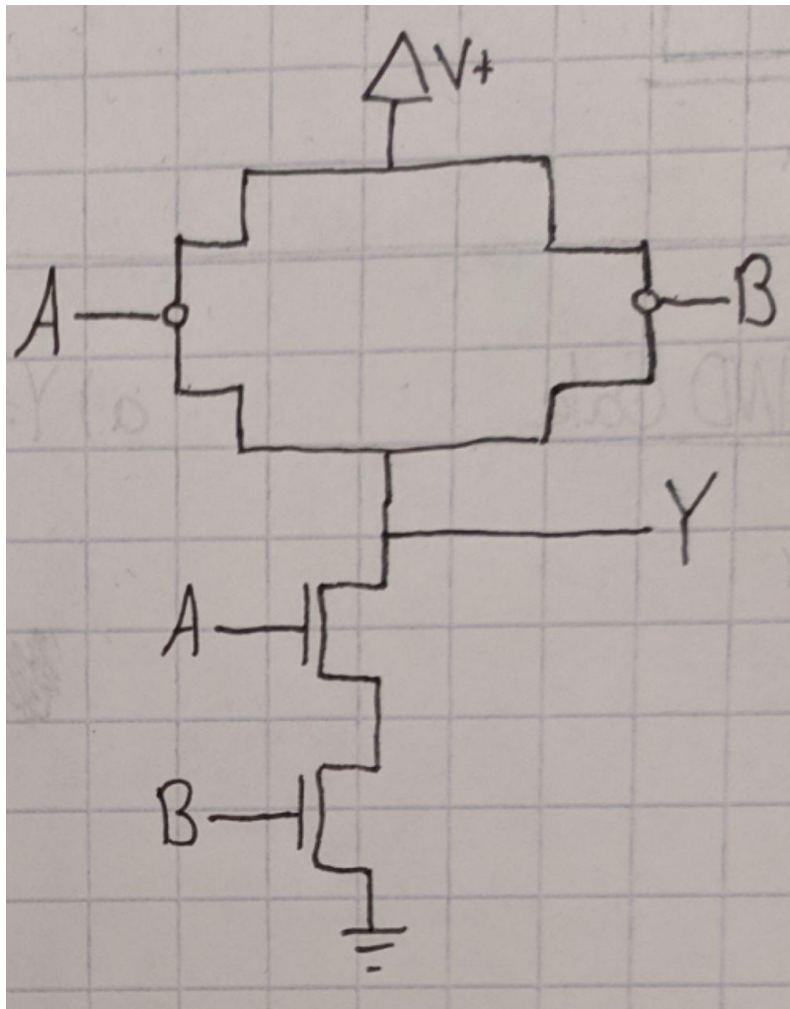


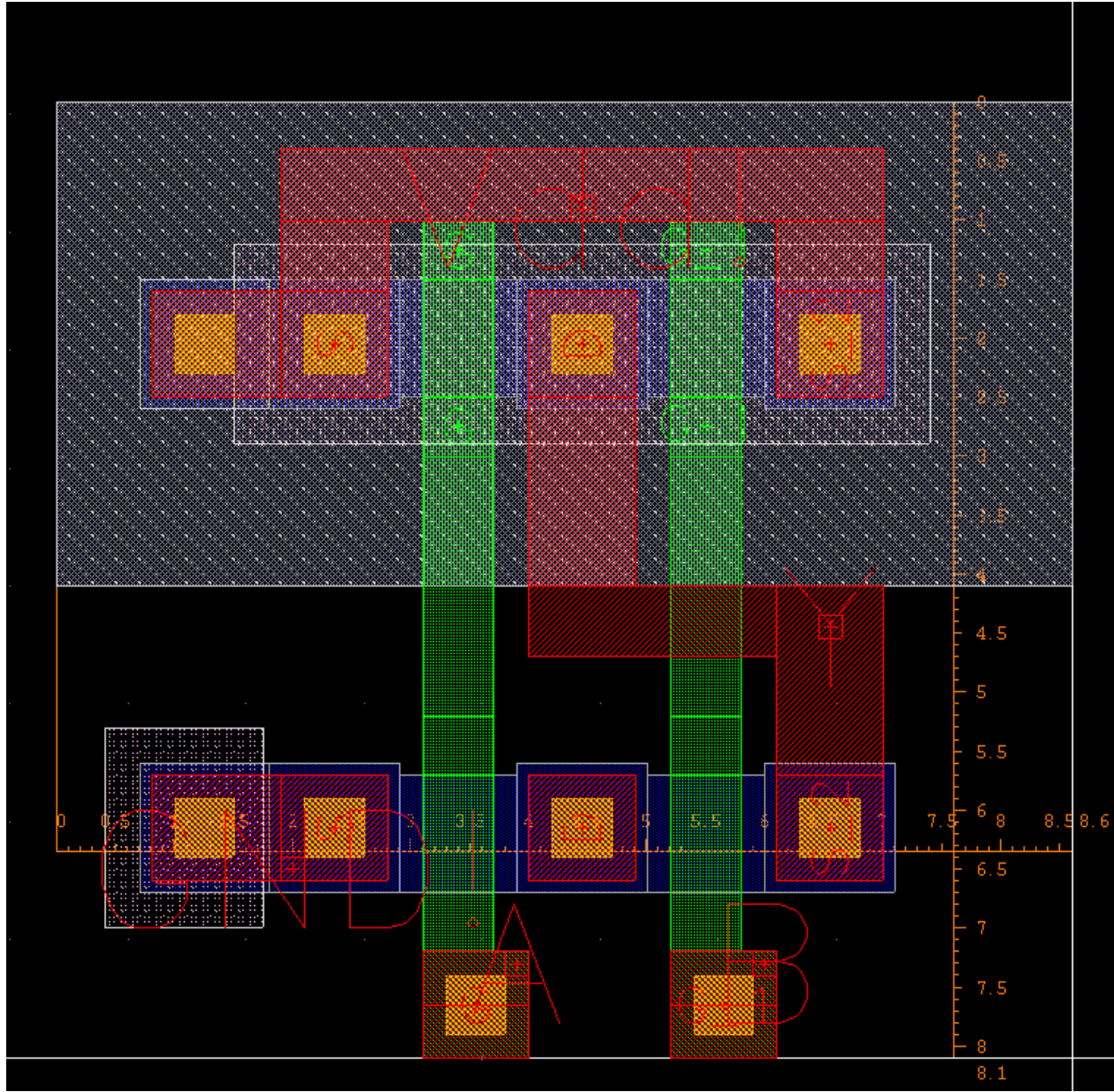


Image of layout -



Bounding box area -

$$8.1 * 8.6 = 69.66$$

## Waveform results -

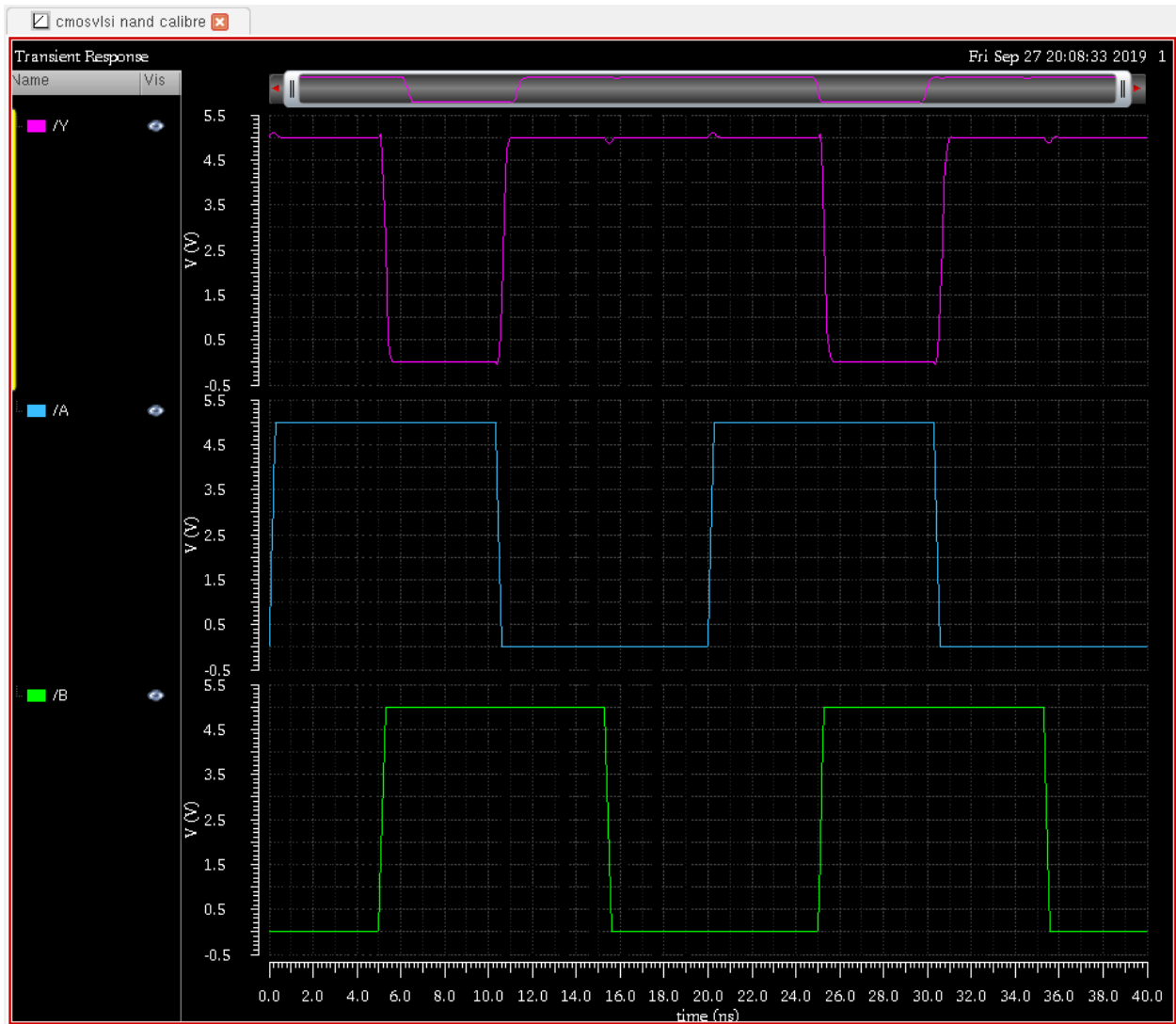


### Question 3 (10 pts): 2-input NOR

Include the following

- a) Transistor level diagram
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

#### Transistor level diagram -

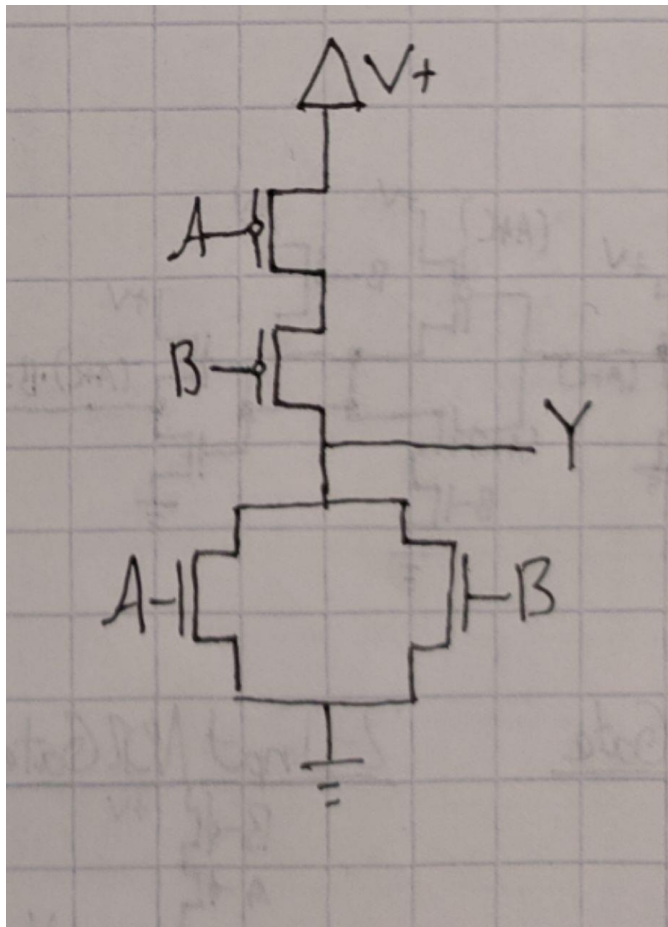



$$8.1 * 8.6 = 69.23$$

$$8.1 * 8.6 = 69.23$$

## Waveform results -

