

CDA 4213 001/CIS 6930 012
Fall 2019
CMOS VLSI Design

Lab 4 Report

Canvas Submission
Due: 11:59 PM, 6th Oct. 2019

You need to submit only report for your team.

Note: Upload PDF version of this report. Only PDF format is accepted.


Today's Date:	10-11-19
Your Team and U Numbers:	Trent Callahan - U14228486 Denislav Tsonev - U64519666 Boyang Wu - U95035892
Your U Number:	U14228486
No. of Hours Spent:	18
Exercise Difficulty: (Easy, Average, Hard)	Average
Work Distribution: (Identify who did what)	Denislav - XOR Gate, optimization Boyang - Full Adder, fixed/optimized oscillator Trent - Initial oscillator, lab report
Any Other Feedback:	

Question 1 (5 pts): 2-input XOR


Include the following

- a) Transistor level diagram
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

Transistor Level Diagram -

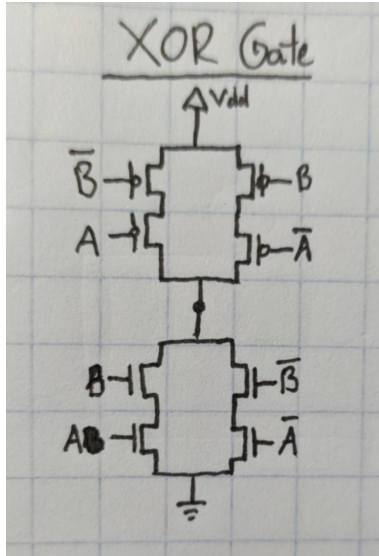

Layout Image -

 


Bounding Box Area -

$$23.15 \times 22.8 = 527.82$$

Total area is **527.82**.

Waveform Results -

 


Question 2 (10 pts): Full Adder


Include the following

- Transistor level diagram
- Image of your layout
- Bounding box area (width x height)
- Waveform results

Transistor Level Diagram -

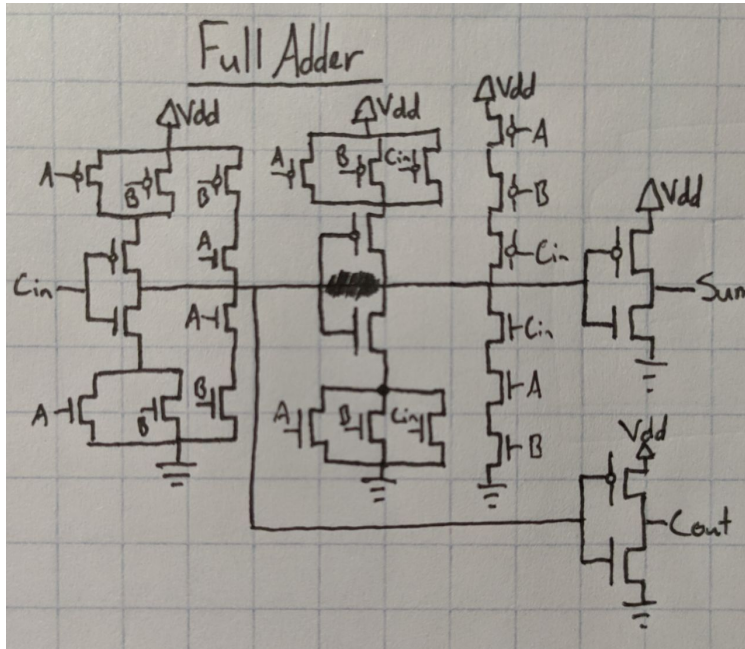

Layout Image -

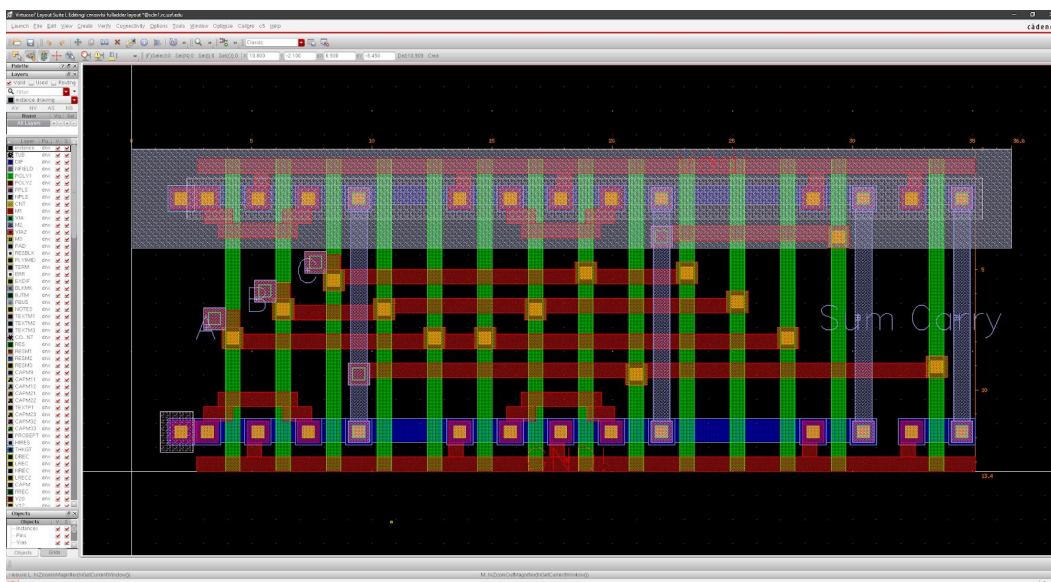

Bounding Box Area -

$$36.6 \times 13.4 = 490.44$$

Total area is **490.44**.

Waveform Results -



Question 3 (5 pts): 15-stage Ring Oscillator


Include the following

- a) Clock frequency of the ring oscillator
- b) Image of your layout
- c) Bounding box area (width x height)
- d) Waveform results

Clock Frequency -

Assuming roughly 7ns per cycle, the oscillator operated at a ~142MHz frequency.

Layout image -

 

Bounding Box Area -

$$80.1 \times 7.8 = 624.78$$

Total area is **624.78**.

Waveform Results -

